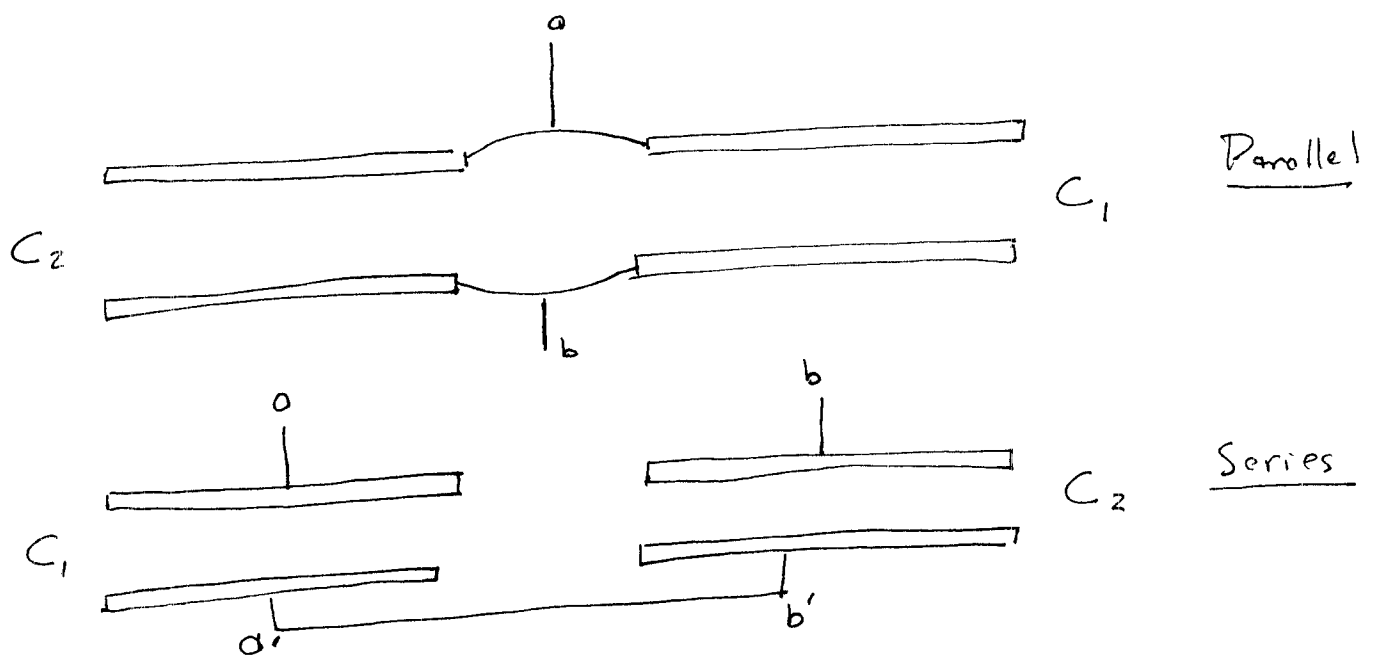


## Capacitance II

Adding capacitors Once again consider our parallel-plate capacitor. We can connect two parallel-plate systems together in two different ways.



Let each capacitor have plate area  $A$  and separation  $d$ . The capacitance of the individual capacitors are  $C_i = \frac{\epsilon_0 A}{d}$

If we place  $Q_a = +Q$  and  $Q_b = -Q$  on the parallel combination, the charge divides between the two capacitors. The charge divides in such a way as to equalize the potential differences.

Let  $\Delta V_{eq}$  be the final potential difference. This must be the same potential difference as the individual capacitors. (2)

$$\Delta V_{eq} = \Delta V_1 = \Delta V_2$$

Using definition of capacitance,

$$Q_1 = C_1 \Delta V_1 \quad Q_2 = C_2 \Delta V_2$$

$$Q = Q_1 + Q_2 = C_1 \Delta V_1 + C_2 \Delta V_2 \\ = (C_1 + C_2) \Delta V_{eq}$$

$$C_{eq} = \frac{Q}{\Delta V_{eq}} = C_1 + C_2 \quad \text{Parallel}$$

Series For the series combination, if  $+Q$  is placed on plate A,  $-Q$  is drawn to plate a' leaving  $+Q$  on plate b' which balances a charge  $-Q$  placed on b.

Now, the total charge on each capacitor is the same

$$Q_{eq} = Q_1 = Q_2$$

The total potential difference is the sum of the potential differences

$$\Delta V = \Delta V_1 + \Delta V_2$$

$$= \frac{Q_1}{C_1} + \frac{Q_2}{C_2} = Q_{eq} \left( \frac{1}{C_1} + \frac{1}{C_2} \right)$$

$$C_{eq} = \frac{Q_{eq}}{\Delta V} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$


$$\boxed{\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}}$$

Series capacitors.

③

So let's start adding some more interesting combinations

4

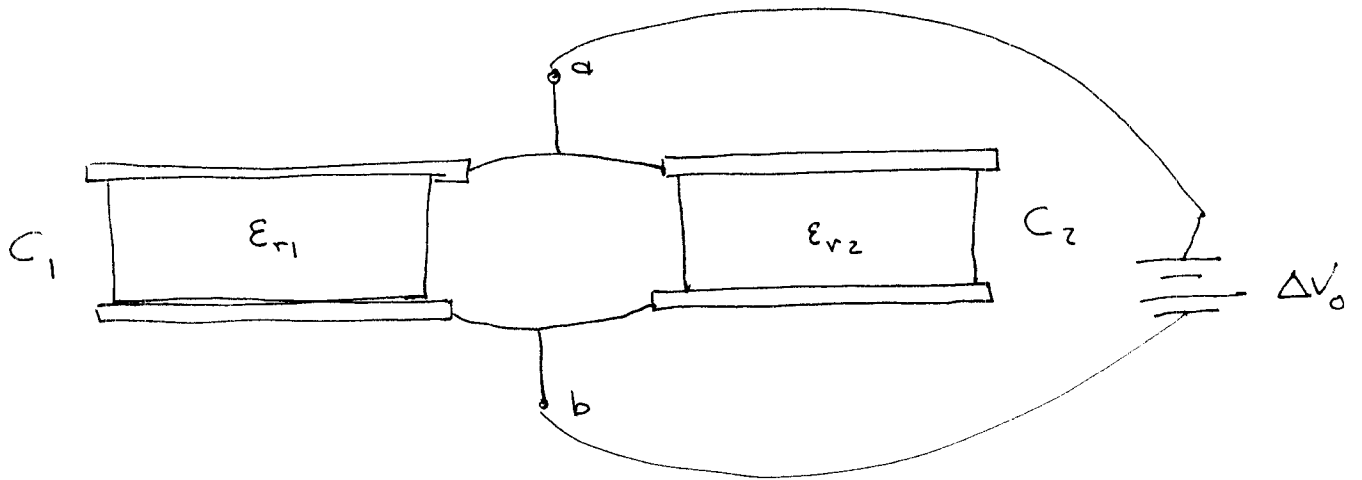

Let  $C_0 = \frac{A\epsilon_0}{d}$  be air-filled capacitance.

$$C_1 = \epsilon_{r1} C_0$$

$$C_2 = \epsilon_{r2} C_0$$

$$\Delta V_1 = \Delta V_2 = \Delta V_0$$


$$E_1 = E_2 = \frac{\Delta V_0}{d}$$

$$\sigma_1 = \frac{Q_1}{A} = \frac{C_1 \Delta V_1}{A} = \epsilon_{r1} \frac{C_0 \Delta V_0}{A}$$

$$\sigma_2 = \epsilon_{r2} \frac{C_0 \Delta V_0}{A}$$

Slide the two plates together

5

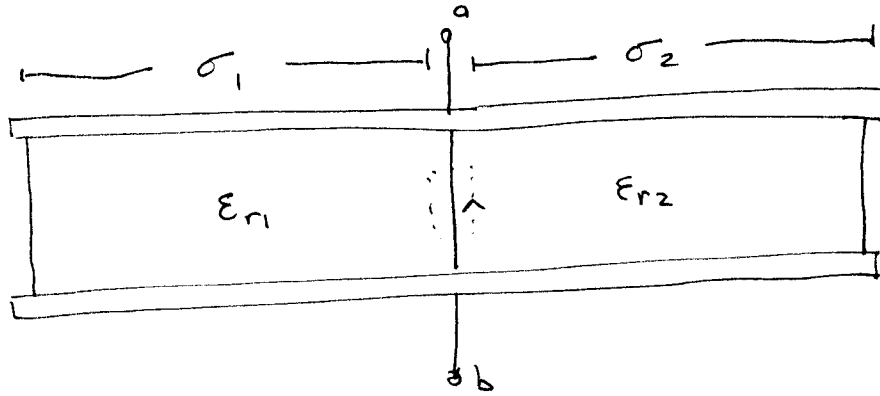

We must have the same system. Check boundary conditions.



$$\vec{E}_1 \cdot \hat{n} = 0 = \vec{E}_2 \cdot \hat{n}$$

$$\vec{E}_1 \cdot \hat{t} = \vec{E}_2 \cdot \hat{t} \quad \text{since} \quad \vec{E}_1 = \vec{E}_2$$

$$C_{eq} = C_1 + C_2$$

Note, different charge densities above the two dielectrics.



Like wise

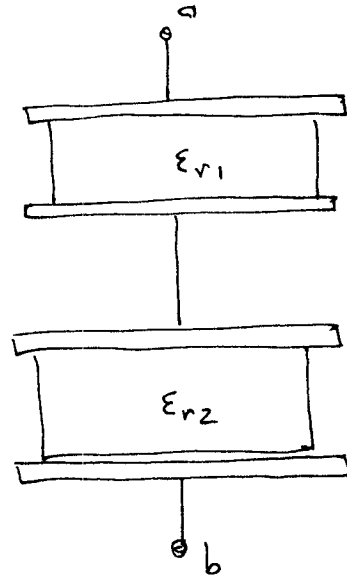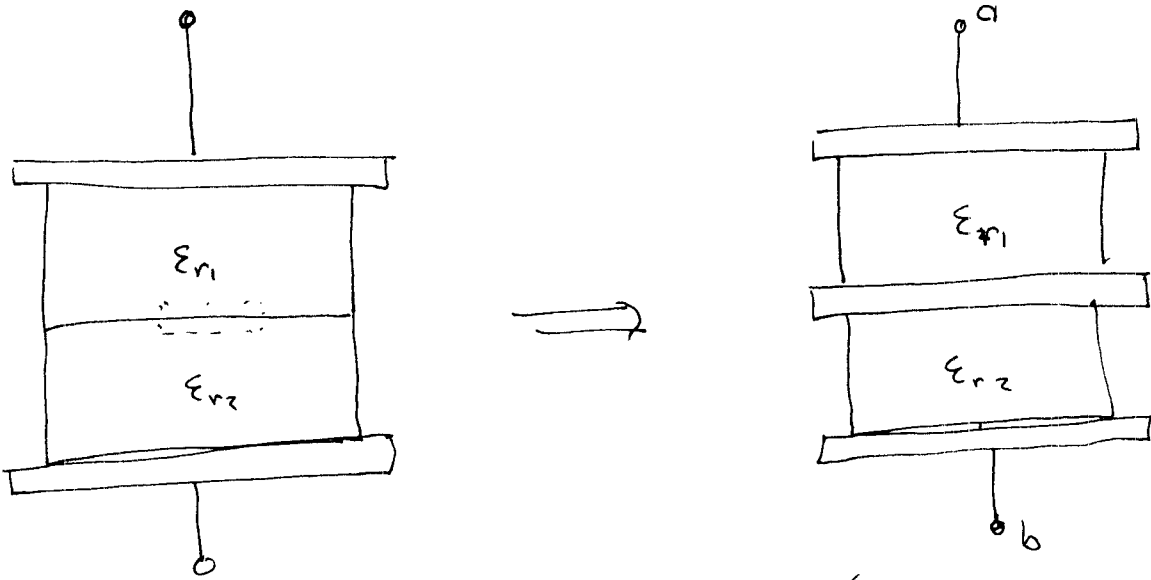

$$\frac{1}{C_{ab}} = \frac{1}{C_1} + \frac{1}{C_2}$$

Now,  $\Delta V_{ab} = \Delta V_1 + \Delta V_2$

Next trick

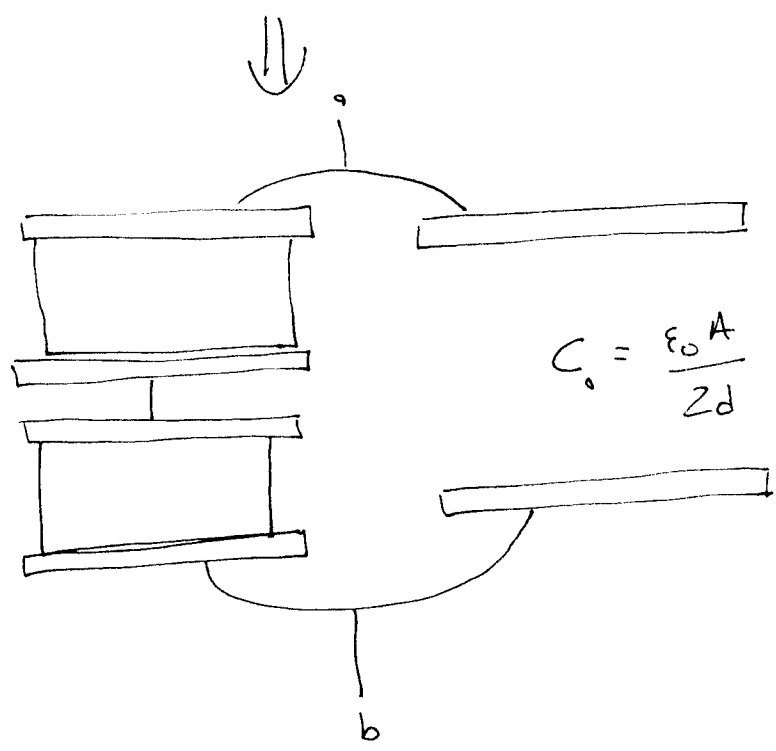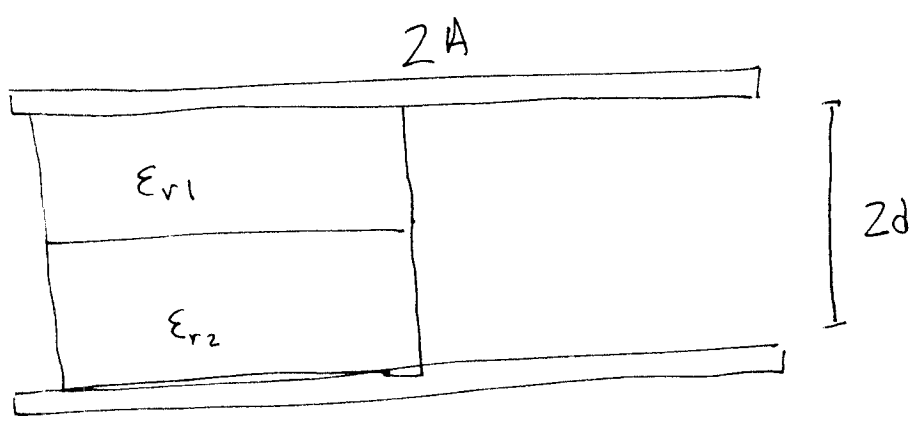

$$E_0 = \frac{\Delta V}{2d}$$

$$\frac{1}{C_{12}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$Q_{12} = C_{12} \Delta V$$

$$\Delta V_1 = \frac{Q_{12}}{C_1}$$

$$\Delta V_2 = \frac{Q_{12}}{C_2}$$

$$E_1 = \frac{\Delta V_1}{d}$$


$$E_2 = \frac{\Delta V_2}{d}$$

Note, we no longer meet electrostatic boundary conditions

$$E_1 \neq E_2 \neq E_0$$

so we have to make the approximation that the fringing field is small.

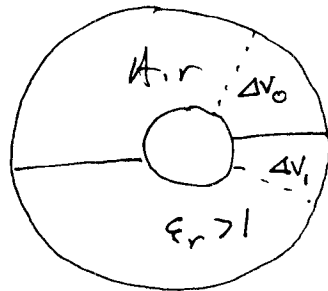⇒ If we do meet the electrostatic boundary conditions the solution is exact. For example,



cylinder


$$\Delta V_0 = \Delta V_1 \Rightarrow E_1 = E_0 \text{ so boundary conditions are met.}$$

⇒ Different charge densities


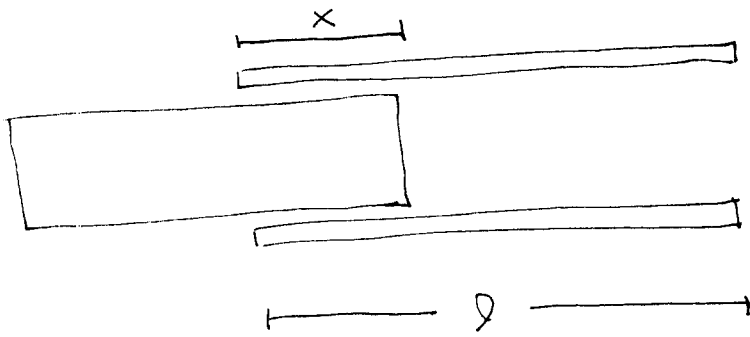
## Force on Capacitors

Consider a dielectric partially inserted into a parallel-plate capacitor.



Let other plate dimension also be  $l$

Two cases

I. Connected to battery ( $\Delta V = \text{constant}$ )

II. Charged then disconnected ( $Q = \text{constant}$ )

Case II  $Q = \text{constant}$

$$F = -\frac{dW}{dx} = -\frac{d}{dx} \frac{Q^2}{2C} = -Q^2 \frac{dC^{-1}}{dx}$$

$$= \frac{1}{2} \frac{Q^2}{C^2} \frac{dC}{dx}$$

The two halves of the capacitor are in parallel

$$C = C_1 + C_2$$

$$= \epsilon_r \frac{\epsilon_0 l x}{d} + \frac{\epsilon_0 l (l-x)}{d} = C_0 \left( \epsilon_r \frac{x}{l} - \frac{x}{l} + 1 \right)$$

$$= \frac{\epsilon_0 l}{d} \left( \epsilon_r x + l - x \right) = C_0 \left( (\epsilon_r - 1) \frac{x}{l} + 1 \right)$$

$$\frac{dC}{dx} = \frac{(\epsilon_r - 1) \epsilon_0 l}{d} = \frac{C_0}{l} (\epsilon_r - 1)$$

$$F = \frac{1}{2} \frac{Q^2}{C^2} \frac{dC}{dx} = \frac{Q^2}{2C_0^2 \left( (\epsilon_r - 1) \frac{x}{l} + 1 \right)} \cdot \frac{C_0}{l} (\epsilon_r - 1)$$

$$= \frac{Q^2}{2C_0 l} \frac{\epsilon_r - 1}{(\epsilon_r - 1) \frac{x}{l} + 1}$$

Case I  $\Delta V$  constant

Two sources of energy - Energy stored in capacitor and energy delivered by battery.

I. Capacitor  $dW = \frac{1}{2} C (\Delta V)^2$

$$\frac{dW}{dx} = \frac{(\Delta V)^2}{2} \frac{dC}{dx}$$

II Battery  $dW = -V dQ$

(- because battery loses energy)

$$= -V (V dC)$$

$$\frac{dW}{dx} = -V^2 \frac{dC}{dx}$$

As before,

$$C = C_0 \left( (\epsilon_r - 1) \frac{x}{d} + 1 \right)$$

$$F = -\frac{dW}{dx} = -\frac{1}{2} v^2 \frac{dc}{dx} + v^2 \frac{dc}{dx}$$

$$= \frac{v^2 dc}{2 dx} = \frac{C_0 v^2 (\epsilon_r - 1)}{2D}$$